


by Tony R. Kuphaldt (2008)

Ladder-style diagrams make PLC I/O documentation very easy to create and to understand. This tutorial provides some blank template pages for you to use in creating your own ladder diagrams for documenting PLC-controlled systems, as well as giving practical examples of what these diagrams can and should look like.

[illegible]


1

An easy way to introduce a PLC into a ladder circuit diagram is to show the discrete input and output cards as boxes. Input I/O points, which receive power from external switches and therefore act as loads, are drawn on the right-hand side of a ladder diagram just as relay coils and lamps are. The “common” terminal(s) connect to the right-hand power bus while the individual input terminals receive power through input switches from the left-hand power bus:

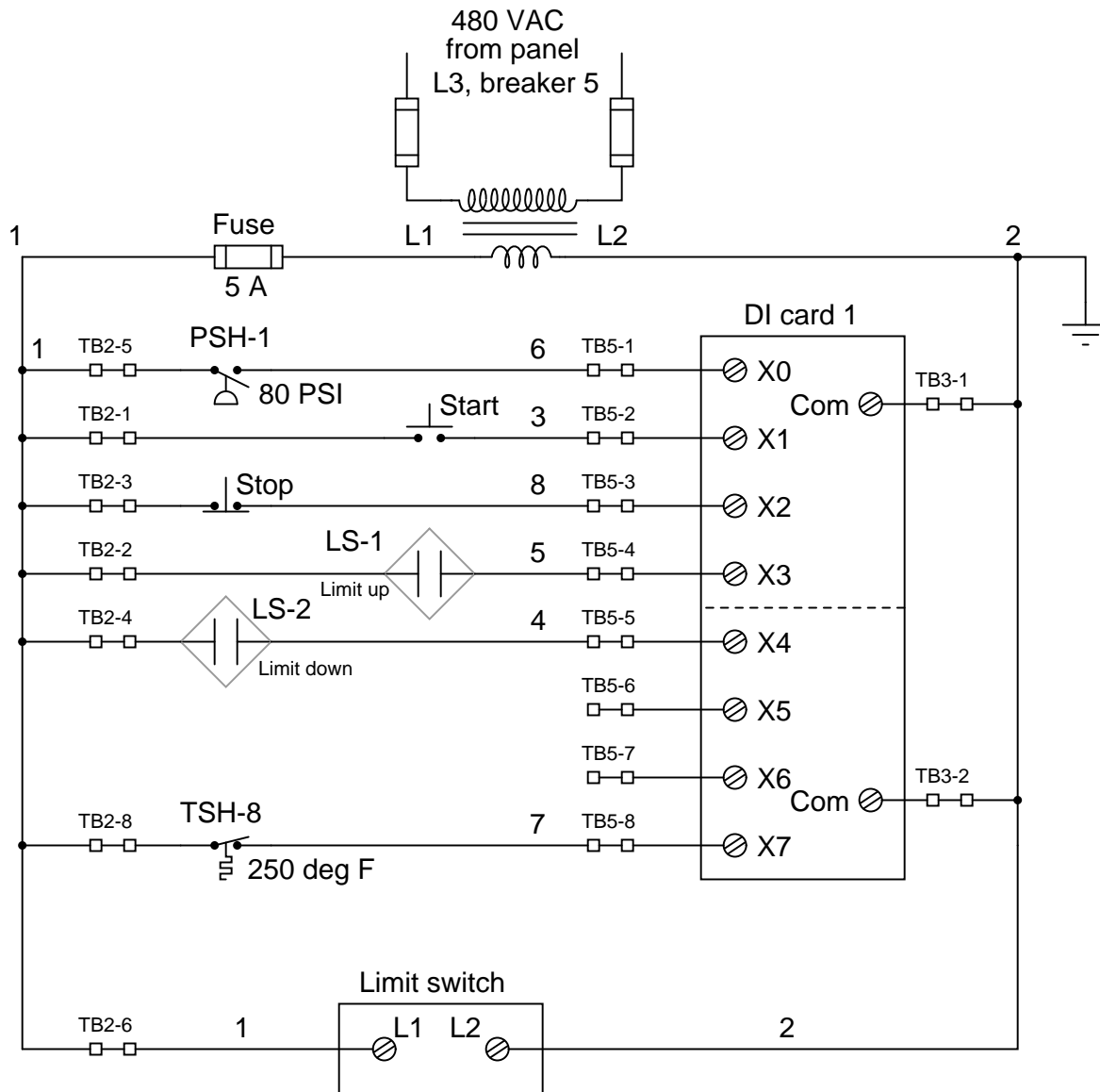


If the inputs of a PLC are 24 VDC instead of 120 VAC, the ladder diagram need only be altered at the very top, showing the two power bus lines coming from a 24 VDC power supply instead of a control power transformer. All other conventions and diagram layout styles remain the same.

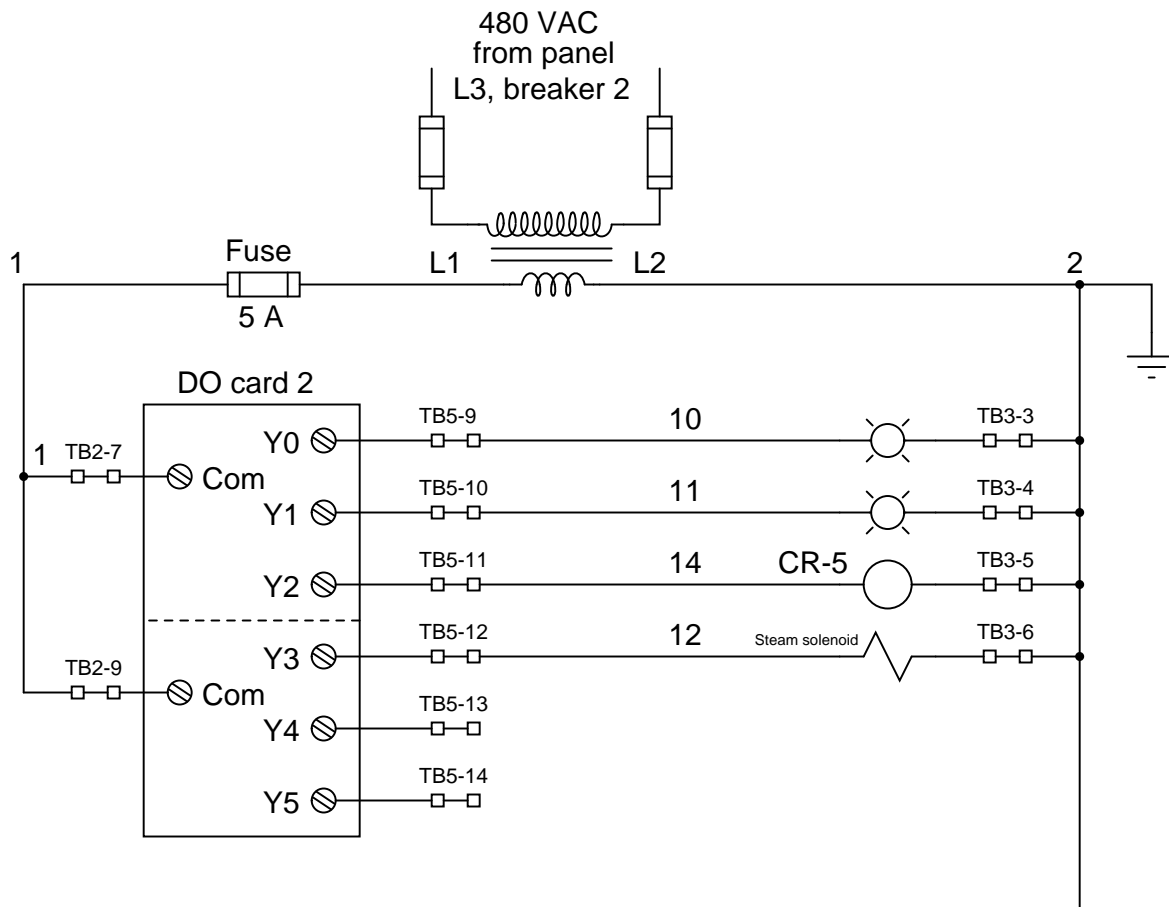
Output I/O points, which send power to load devices, are drawn on the left-hand side of a ladder diagram just as switches are:



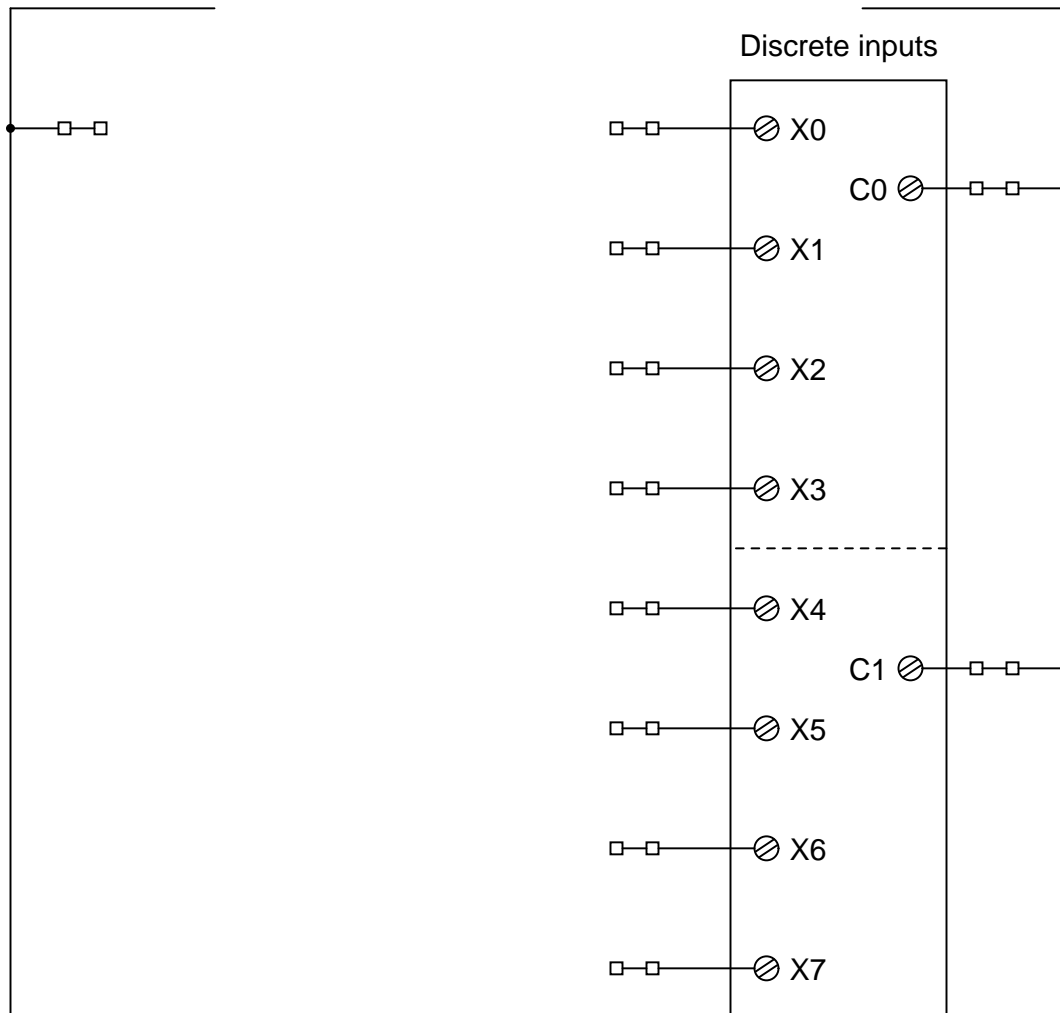As you can see, the convention of ladder diagrams makes PLC I/O documentation easy both to create and to interpret, which in turn makes the system much easier to maintain!



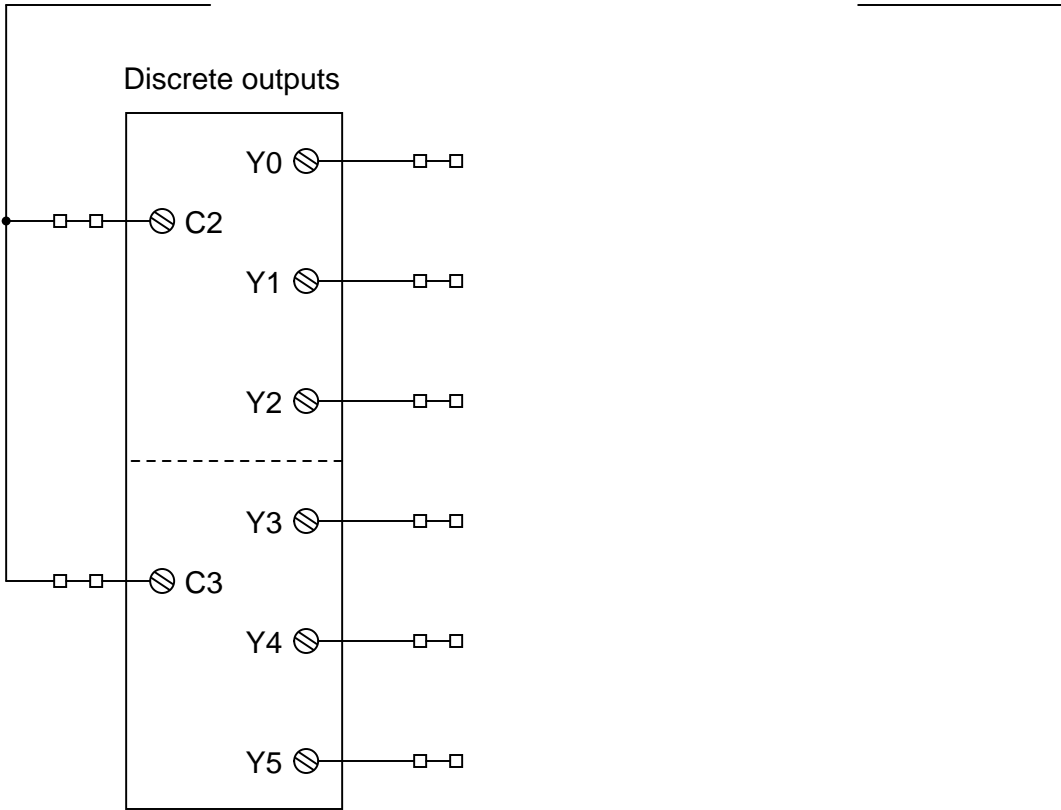PLC output ladder diagram template
(For Automation Direct DL05 PLCs)



Colophon

This document is licensed under the Creative Commons Attribution License, version 1.0. To view a copy of this license, visit <http://creativecommons.org/licenses/by/1.0/>, or send a letter to Creative Commons, 559 Nathan Abbott Way, Stanford, California 94305, USA. The terms and conditions of this license allow for free copying, distribution, and/or modification of all licensed works by the general public.